

DC coupling (most cases)

↓  
measuring voltage.

AC coupling → remove average value

triggers level → most of times is in between  
if unknown level → set above the starting level.

AC: phase shifts. ( $0 \rightarrow 2\pi$ )  
frequency; amplitude - phase.

An AC circuit is only linear component.  
↳ All component has the same frequency  
and sinusoidal wave.

Ex 2.7.

$$v_c(t) = 100 \cos(200t) \quad \omega = 200.$$

$$C: 100 \mu F$$

$$Z_C = \frac{1}{\omega C} \angle -90^\circ = \frac{1}{200 \times 100 \times 10^{-6}} \angle -90^\circ = 50 \angle -90^\circ = 0 - j50$$

$$I_C = \frac{V_C}{Z_C} = \frac{100 \angle 0^\circ}{50 \angle -90^\circ} = 2 \angle 90^\circ = 2 + j0$$


$$V_C = 100 \angle 0 = 100.$$

$$v_R(t) = 100 \cos(200t) \quad \text{to } R.$$

$$Z_R = R = 50.$$

$$Z_R = \frac{V_R}{I_R} = \frac{100}{50} = 2 \angle 0^\circ.$$

$$V_R = 100 \angle 0^\circ.$$

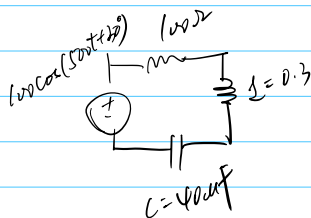

$$Z_L = \omega L \angle 90^\circ = 150 \angle 90^\circ = 0 + j150$$

$$Z_C = \frac{1}{\omega C} \angle -90^\circ = 50 \angle -90^\circ = 0 - j50$$

$$Z_R = 100 \angle 0^\circ = 100 + j0$$

$$Z_{eq} = 100 + j100 = 141 \angle 45^\circ.$$

$$V_s = 100 \angle 30^\circ.$$

$$V_L = Z_L I$$

$$= 150 \angle 90^\circ \cdot 0.33 \angle 30^\circ$$

$$= 50 \angle 120^\circ$$

$$I_s = \frac{V_s}{Z_{eq}} = \frac{100 \angle 30^\circ}{141 \angle 45^\circ} = 0.707 \angle -15^\circ.$$

$$I_s = 0.707 \cos(500t - 15^\circ)$$



$$\begin{aligned}
 V_L &= Z_L I \\
 &= 50 \angle 90^\circ \times 0.707 \angle 30^\circ \\
 &= 35.4 \angle 120^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_R &= R I = 100 \times 0.707 \angle -45^\circ = 70.7 \angle -45^\circ \\
 V_L &= Z_L I = 150 \angle 90^\circ \times 0.707 \angle -15^\circ = 106 \angle 75^\circ \\
 V_C &= Z_C I = 50 \angle -90^\circ \times 0.707 \angle -15^\circ = 35.4 \angle -105^\circ
 \end{aligned}$$

$$V_R = 70.7 \cos(500t - 15^\circ)$$

$$V_L = 106 \cos(500t + 75^\circ)$$

$$V_C = 35.4 \cos(500t - 105^\circ)$$

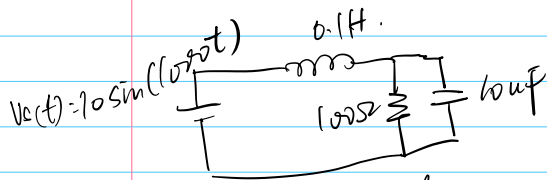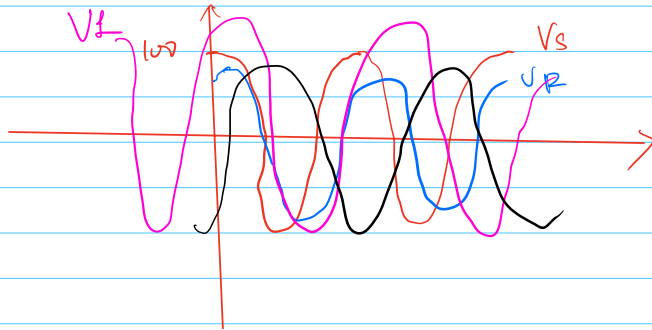

$$I = \frac{V}{Z_{eq}} = \frac{10 \angle 0^\circ}{70.71 \angle 45^\circ} = 0.141 \angle -45^\circ$$

$$\begin{aligned}
 V_L &= Z_L I = 100 \angle 90^\circ \times 0.141 \angle -45^\circ \\
 &= 14.1 \angle 45^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_C &= Z_C I = 70.71 \angle -45^\circ \times 0.141 \angle -45^\circ \\
 &= 10 \angle -90^\circ
 \end{aligned}$$

$$\bar{V}_s = 10 \angle -90^\circ$$

$$\bar{I}_R = \frac{\bar{V}_C}{R} = \frac{10 \angle -180^\circ}{100 \angle 0^\circ} = 0.1 \angle -180^\circ$$

$$\bar{I}_C = \frac{\bar{V}_R}{Z_C} = \frac{10 \angle -180^\circ}{10 \angle -90^\circ} = 0.1 \angle -90^\circ$$

$$\bar{V}_s = 10 \angle 0^\circ$$

$$\bar{Z}_L = j\omega L = j100$$

$$\bar{Z}_C = \frac{1}{j\omega C} = -j100$$

$$R = 100 + j0$$

$$\bar{Z}_{eq} = \bar{Z}_L + \bar{Z}_{RC}$$

$$\bar{Z}_{RC} = \frac{\bar{Z}_R \times \bar{Z}_C}{\bar{Z}_R + \bar{Z}_C}$$

$$= \frac{100 \angle 0^\circ \times 100 \angle -90^\circ}{100 \angle 0^\circ - 100 \angle 90^\circ}$$

$$= \frac{10000 \angle -90^\circ}{200 \angle -45^\circ}$$


$$= 50 \angle -45^\circ$$

$$\bar{Z}_{eq} = \bar{Z}_L + \bar{Z}_{RC}$$

$$= 0 + j100 + 50 - j50$$

$$= 50 + j50$$

$$= 70.71 \angle 45^\circ$$

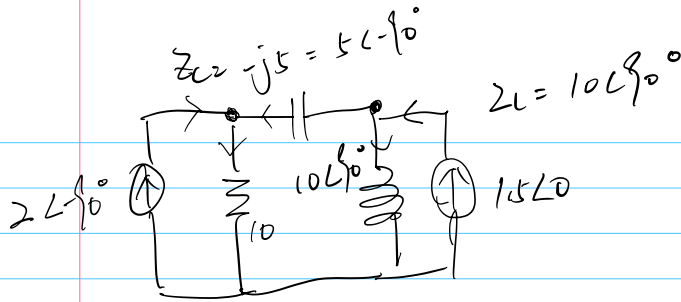

$$\frac{\bar{V}_1}{10} = 2\angle-90^\circ + \frac{\bar{V}_2 - \bar{V}_1}{Z_c}$$

$$\frac{\bar{V}_1}{10} + \frac{\bar{V}_1 - \bar{V}_2}{Z_c} = 2\angle-90^\circ$$

$$\frac{\bar{V}_2 - \bar{V}_1}{Z_c} + 1.5\angle 0 = \frac{\bar{V}_2}{Z_L}$$

$$\frac{\bar{V}_2}{Z_L} + \frac{\bar{V}_2 - \bar{V}_1}{Z_c} = 1.5\angle 0. \quad Z_c \bar{V}_2 + Z_L (\bar{V}_2 - \bar{V}_1) = 1.5\angle 0 (Z_L + Z_c)$$

$$\frac{\bar{V}_1}{10} + \frac{\bar{V}_1}{Z_c} - \frac{\bar{V}_2}{Z_c} = 2\angle-90^\circ$$

$$(10 - j5) \bar{V}_2 - \bar{V}_1 = 75$$

$$0.1\bar{V}_1 + 0.2j\bar{V}_1 - 0.2j\bar{V}_2 = j2$$

$$(0.1 + 0.2j)\bar{V}_1 - 0.2j\bar{V}_2 = j2$$

$$-0.1j\bar{V}_2 + 0.2j\bar{V}_2 - 0.2j\bar{V}_1 = 1.5$$

$$0.1j\bar{V}_2 - 0.2j\bar{V}_1 = 1.5$$

$$0.2j\bar{V}_2 - 0.4j\bar{V}_1 = 3$$

$$0.1 - j0.2\bar{V}_1 = 3 - j2$$

$$\bar{V}_1 = \frac{3 - j2}{0.1 - j0.2}$$

$$= \frac{\sqrt{13} \angle -33.69^\circ}{\sqrt{0.05} \angle -63.43^\circ}$$

$$= \frac{\sqrt{13}}{\sqrt{0.05}} \angle 29.7^\circ$$

8-0

$$V_1 = 16.1 \cos(100t + 29.7^\circ)$$

$$= 16.1 \angle 27.1^\circ$$

$$V_L = L \frac{di}{dt}$$

A.

$$10i + V_L = V_S$$

$$10i + L \frac{di}{dt} = V_S$$

$$\frac{di}{dt} + 100i = 100 \sin(100t) \quad i = L \frac{dV_C}{dt}$$

$$10i + V_C = V_S$$

$$100 \frac{dV_C}{dt} + V_C = 10 \sin(10^4 t)$$

$$10 \times 100 \times 10^{-6} \frac{dV_C}{dt} + V_C = 10 \sin(10^4 t)$$

$$\frac{dV_C}{dt} + 1000 V_C = 10000 \sin(10^4 t)$$

$$B-1) \bar{V}_1 = 20 \angle \frac{\pi}{5}$$

$$B-2) \bar{V}_2 = 150 \sin(\omega t + \pi) = 50 \angle \pi$$

$$B-3) \bar{V}_3 = 200 \angle \frac{\pi}{2}$$

$$B-4) \bar{I}_1 = 100 \angle -\frac{\pi}{3}$$

$$B-5) \bar{I}_2 = 5 \cos(\omega t - \frac{\pi}{4} + \pi) = 5 \cos(t + \frac{3}{4}\pi) = 5 \cos(t + \frac{5}{4}\pi) = 5 \angle \frac{5\pi}{4}$$

$$B-6) \bar{I}_3 = 50 \angle \frac{\pi}{4}$$

$$C-1) v_1 = 100 \sin(\omega t + \frac{\pi}{4})$$

$$C-2) v_2(t) = 200 \sin(\omega t)$$

$$C-3) v_3(t) = 10 \sin(\omega t - \frac{\pi}{4})$$

$$C-4) i_1(t) = 0.1 \sin(\omega t - \frac{\pi}{6})$$

$$C-5) i_2(t) = 1.5 \sin(\omega t - \frac{\pi}{6})$$

$$C-6) i_3(t) = 0.42 \sin(\omega t + \frac{\pi}{3})$$

$$D-i) \bar{Z} = R + jX$$

$$= 100 + j\omega L$$

$$= 100 + j0.1002\omega$$

$$D-ii) \bar{Z} = R + jX$$

$$= 100 + j\omega L + j\frac{1}{\omega C}$$

$$= 100 + j0.1\omega + j\frac{1}{1000\omega}$$

$$= 100 + j(0.1\omega - 1000\omega^{-1})$$

$$\begin{aligned}
 \text{Dii)} \quad Z &= R + jX \\
 &= 100 + j - \frac{1}{\omega C} \\
 &= 100 + j - \frac{1}{100 \times 10^{-6} \times 10} \\
 &= 100 - j10000 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{Div)} \quad Z &= R + jX \\
 &= 0 + j0.002\omega - j10000\omega^{-1}
 \end{aligned}$$

D-2

$$\begin{aligned}
 \text{i)} \quad \frac{1}{Z_{eq}} &= \frac{1}{R} + \frac{1}{Z_L} \\
 &= \frac{1}{100} + \frac{1}{j100} \\
 &= \frac{j100 + 100}{100 \times j100} \\
 &= \frac{100 + j100}{10000 \times 100 \angle 90^\circ} \\
 &= \frac{\sqrt{20000} \angle 45^\circ}{1000000 \angle 90^\circ} \\
 &= \frac{10000 \angle 90^\circ}{\sqrt{20000} \angle 45^\circ} \\
 &= 70.7 \angle \frac{\pi}{4}
 \end{aligned}$$

$$\begin{aligned}
 \text{ii)} \quad \frac{1}{Z_{eq}} &= \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \\
 &= \frac{1}{100} + \frac{1}{j100} - j100(100 \times 10^{-6}) \\
 &= \frac{\sqrt{20000} \angle 45^\circ}{10000} - j0.01 \\
 &= 0.01 + j0.01 - j0.01 \\
 &= 0.01 \\
 &= 100 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{iii)} \quad \frac{1}{Z_{eq}} &= \frac{1}{R} + \frac{1}{Z_C} \\
 &= \frac{1}{100} - j\omega C \\
 &= \frac{1}{100} - j100(100 \times 10^{-6}) \\
 &= 0.01 - j0.01 \\
 &= 0.0141 \angle -45^\circ \\
 &= 70.71 \angle -45^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{iv)} \quad \frac{1}{Z_{eq}} &= \frac{1}{Z_R} + \frac{1}{Z_C} \\
 &= \frac{1}{j100} - j^{100 \times 100 \times 10^{-6}} \\
 &= \frac{1}{j100} - j0.01 \\
 &= 0.01 \angle 90^\circ - 0.01 \angle 90^\circ \\
 \frac{1}{Z_{eq}} &= 0. \\
 Z_{eq} &= \frac{1}{0} \rightarrow \infty.
 \end{aligned}$$

D-3

$$\begin{aligned}
 Z_{AB} &= \frac{1}{10 + j10} + \frac{1}{10} \\
 &= \frac{1 \angle 0}{\sqrt{200} \angle 45^\circ} + 0.1
 \end{aligned}$$



$$\begin{aligned}
 &= \frac{1}{\sqrt{200}} \angle -45^\circ + 0.1 \angle 0 \\
 &= 0.05 - j0.05 + 0.1 \\
 &= 0.15 - j0.05 \\
 &= 0.158 \angle -18.43 \\
 &= 6.32 \angle 0.32 \text{ rad } \Omega.
 \end{aligned}$$

$$\begin{aligned}
 \text{ii)} \quad \frac{1}{Z_{AB}} &= \frac{1}{10 + j10} - \frac{1}{j10} \\
 &= \frac{1 \angle 0}{\sqrt{200} \angle 45^\circ} - \frac{1 \angle 0}{10 \angle 90^\circ} \\
 &= \frac{1}{\sqrt{200}} \angle -45^\circ - 0.1 \angle -90^\circ \\
 &= 0.05 - j0.05 - (-j0.1) \\
 &= 0.05 + j0.05 \\
 &= 0.0707 \angle 45^\circ \\
 &= 14.1 \angle -45^\circ = 14.1 \angle -\frac{\pi}{4}.
 \end{aligned}$$

$$\begin{aligned}
 \text{iii)} \quad Z_{eq} &= R + Z_L \\
 &= 10 + j\omega L \\
 &= 10 + j100(100 \times 10^{-3}) \\
 &= 10 + j10 \\
 &= 14.14 \angle 45^\circ \\
 &= 10\sqrt{2} \angle \frac{\pi}{4}.
 \end{aligned}$$

$$\begin{aligned}
 \text{iv)} \quad f &= 50 \text{ Hz} \quad \omega = 2\pi f = 314.2 \text{ rad/s} \\
 Z_{AB} &= R + Z_L + Z_C \\
 &= 30 + j314 \times 0.1 - j \frac{1}{314(100 \times 10^{-6})} \\
 &= 30 + j31.4 - j31.8 \\
 &= 30 + j - 0.45
 \end{aligned}$$

$$= \sqrt{909.17} \angle -0.79^\circ$$

$$= 30 \angle -0.01 \text{ rad } \Omega.$$

v)  $f = 50 \text{ Hz}$      $\omega = 2\pi f = 314.2$

$$\frac{1}{Z_{eq}} = \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C}$$

$$= 0.02 + \frac{1}{j314.2(0.001)} - j314.2 \times 10^{-3}$$

+

$$= 0.02 + \frac{1 \angle 0}{0.314 \angle 90^\circ} - j3.142$$

$$= 0.02 + 3.18 \angle 90^\circ - j3.142$$

$$= 0.02 - j3.18 - j3.142$$

$$= 0.02 - j6.32$$

$$= 6.32 \angle 89.81^\circ$$

$$= 0.158 \angle -1.56 \text{ rad } \Omega.$$

$$= \frac{1}{50} + \frac{1}{j0.314}$$

$$= \frac{50 + j0.314}{50 \times 0.314 \angle 90^\circ}$$

$$= \frac{50 + j0.314}{15.7 \angle 90^\circ}$$

$$= \frac{50 \angle 0.25^\circ}{15.7 \angle 90^\circ}$$

$$= 3.18 \angle -89.64^\circ - j3.14$$

$$= 0.01999 - j3.18 - j3.14$$

$$= 0.01999 - j6.32$$

$$= 6.32 \angle -89.81^\circ$$

$$= 0.158 \angle 89.81^\circ$$

$$= 0.158 \angle 1.56^\circ$$

E. a)  $V_s = 200 \sin(2\pi 50 t)$

$$Z_{eq} = R + Z_L$$

$$= 10 + j\omega L$$

$$= 10 + j2\pi 50(0.1)$$

$$= 10 + j10\pi$$

$$\bar{I}_s = \frac{\bar{V}_s}{Z_{eq}} = \frac{200 \angle 0}{10 + j10\pi}$$

$$Z_s = 1.840 - j5.78$$

$$= 6.07 \angle -1.26$$

$$\hat{i}_s(t) = 6.15 \sin(2\pi 50t - 1.26)$$

$$V_1 = R \hat{I}_s$$

$$= 10.75$$

$$= 60.7 \angle -1.26$$

$$= 61.5 \sin(2\pi 50t - 1.26)$$

$$V_2 = j\omega L \cdot I_s$$

$$= j2\pi 50(0.1) \times 6.07 \angle -1.26$$

$$= 181.06 + j57.805$$

$$= 190.8 \sin(2\pi 50t - 0.308)$$

$$b) \bar{V} = 71 \angle 0 \quad \omega = 100\pi$$

$$\bar{Z}_{eq} = \frac{1}{\frac{1}{10} + j\omega C}$$

$$= 9.101 - j2.85$$

$$= 9.54 \angle -0.304$$

$$\bar{I}_s = \frac{\bar{V}}{\bar{Z}_{eq}} = 7.1 + j2.23$$

$$= 7.44 \angle 0.304$$

$$\bar{i}_1 = \frac{\bar{Z}_C}{R + \bar{Z}_C} \bar{I}_s$$

$$= 7.1 - j3.303$$

$$\bar{i}_2 = \frac{\bar{V}_C}{\bar{Z}_C}$$

$$= \frac{71}{j\omega C}$$

$$= 2.23A$$

$$c) \bar{V}_s = 50$$

$$\bar{Z}_{eq} = \frac{1}{\frac{1}{R + j\omega L} + j\omega C}$$

$$= \frac{1}{\frac{1}{10 + j30} + j0.03}$$

$$= 100$$

$$\hat{i}_s(t) = \frac{V_s}{Z_{eq}} = \frac{50}{100} = 0.5A$$

E-2.

$$Z = 8 + j6 \Omega$$

$$\hat{i}_s(t) = 0.4 - 0.3j$$

$$= 0.5 \angle -0.635$$

Amplitude is 0.5



$$\phi' = -0.64.$$

$$i_s = 5 \sin(100\pi t - \frac{\pi}{8})$$

$$\omega = 100\pi.$$



$$E-3. \quad \bar{I}_s = \frac{V_s}{Z_{eq}}$$

$$Z_{eq} = \frac{V_s}{I_s}$$

$$= \frac{230 \angle 0}{5 \angle -\frac{\pi}{8}}$$

$$= \frac{230 + j0}{4.33 - j1.5}$$

$$= 39.8 + j23$$

$$= 46 \angle 0.524 \text{ rad} \angle \frac{\pi}{6}$$

$$b) \quad Z_{eq} = R + j\omega L$$

$$= 39.8 + j23.$$

$$L = 0.073$$

$$= 73 \text{ mH}$$

E-4. impedance is smallest at resonance.

$$\omega_n = \frac{1}{\sqrt{LC}} = 3162.7$$

$$f = 503 \text{ Hz.}$$