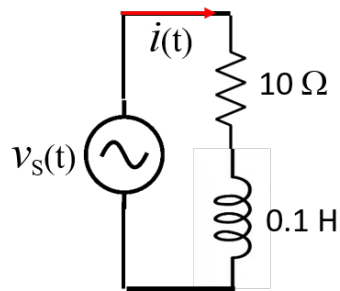


AC Circuit Practice Problems

A. KVL equation in time-domain

- i. Write the time-domain KVL equation (ODE) for the following circuit if

$$v_S(t) = 10 \sin(100t).$$



Answer: $\frac{di}{dt} + 100i = 100 \sin(100t)$

- ii. Write the time-domain KVL equation (ODE) of a series RC circuit keeping capacitor voltage as the unknown variable given that

$$v_S(t) = 10 \sin(10^4 t), C = 100 \mu F, R = 10 \Omega.$$

Answer: $\frac{dv_C}{dt} + 10^3 v_C = 10^4 \sin(10^4 t)$

B. Write the phasor representation of a sinusoidal voltage/ current using the convention

$$A \sin(\omega t + \phi) \Leftrightarrow A e^{j\phi} = A \angle \phi.$$

B-1

$$v_1(t) = 20 \sin\left(\omega t + \frac{\pi}{5}\right) \text{ volt},$$

B-2

$$v_2(t) = -50 \sin(\omega t) \text{ volt},$$

B-3

$$v_3(t) = 200 \cos(\omega t) \text{ volt},$$

B-4

$$i_1(t) = 100 \sin\left(10^4 t - \frac{\pi}{3}\right) \text{ mA},$$

B-5

$$i_2(t) = -5 \cos(\omega t - \frac{\pi}{4}) \text{ A},$$

B-6

$$i_3(t) = 50 \sin(100t + \frac{\pi}{4}) \text{ mA}.$$

Answer:

$$\bar{V}_1 = 20 \angle \frac{\pi}{5} \text{ V}, \bar{V}_2 = 50 \angle \pi \text{ V}, \bar{V}_3 = 200 \angle \frac{\pi}{2} \text{ V},$$

$$\bar{I}_1 = 100 \angle -\frac{\pi}{3} \text{ mA}, \bar{I}_2 = 5 \angle \frac{5\pi}{4} \text{ A or } 5 \angle -\frac{3\pi}{4}, \bar{I}_3 = 50 \angle \frac{\pi}{4} \text{ mA}.$$

C. Convert phasor into time-domain function using the convention

$$A \sin(\omega t + \phi) \Leftrightarrow A e^{j\phi} = A \angle \phi.$$

Use ω as the radian frequency.

C-1

$$\bar{V}_1 = 100 \angle \frac{\pi}{4} \text{ mV},$$

C-2

$$\bar{V}_2 = 200 \angle 0 \text{ V},$$

C-3

$$\bar{V}_3 = 10 \angle -\frac{\pi}{4} \text{ V},$$

C-4

$$\bar{I}_1 = 100 \angle -\frac{\pi}{6} \text{ mA},$$

C-5

$$\bar{I}_2 = 1.5 \angle -\frac{\pi}{6} \text{ A},$$

C-6

$$\bar{I}_3 = 420 \angle \frac{\pi}{3} \text{ mA}.$$

Answer:

$$v_1 = 100 \sin(\omega t + \frac{\pi}{4}) \text{ mV}, v_2 = 200 \sin(\omega t) \text{ V}, v_3 = 10 \sin(\omega t - \frac{\pi}{4}) \text{ V},$$

$$i_1 = 100 \sin(\omega t - \frac{\pi}{6}) \text{ mA}, i_2 = 1.5 \sin(\omega t - \frac{\pi}{6}) \text{ A}, i_3 = 420 \sin(\omega t + \frac{\pi}{3}) \text{ mA}$$

D. Impedance

D-1 Find the equivalent complex impedance for each of the following questions assuming that the components are connected in series. Express your answers in terms of the radian frequency ω :

i.

$$R = 100 \Omega, L = 2 \text{ mH}$$

ii.

$$R = 100\Omega, L = 0.1 H, C = 1000 \mu F$$

iii.

$$R = 100\Omega, C = 100 \mu F$$

iv.

$$L = 2 mH, C = 1000 \mu F$$

Answer:

$$i. 100 + j2 \times 10^{-3} \omega \ \Omega$$

$$ii. 100 + j(0.1\omega - \frac{10^3}{\omega}) \ \Omega$$

$$iii. 100 - j\frac{10^4}{\omega} \ \Omega$$

$$iv. +j(\frac{\omega}{500} - \frac{1000}{\omega}) \ \Omega$$

D-2 Find the equivalent complex impedance for the following questions assuming that the components are connect in parallel. Assume $\omega = 100$ rad/s:

i.

$$R = 100\Omega, L = 1 H$$

ii.

$$R = 100\Omega, L = 1 H, C = 100 \mu F$$

iii.

$$R = 100\Omega, C = 100 \mu F$$


iv.

$$L = 1 H, C = 100 \mu F$$

Answer:


$$i. 70.7\angle\frac{\pi}{4} \ \Omega, \quad ii. 100 \ \Omega, \quad iii. 70.7\angle-\frac{\pi}{4}, \ \Omega, \quad iv. \infty$$

D-3 Find the equivalent impedance Z_{AB} between the points A and B for each of the following:

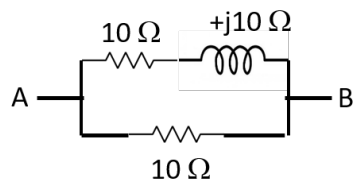i. $Z_{AB} = ?$ **Answer:**

$$Z_{AB} = 6 + j2 \ \Omega = 6.32\angle0.32 \text{ rad} \ \Omega.$$


ii. $Z_{AB} = ?$

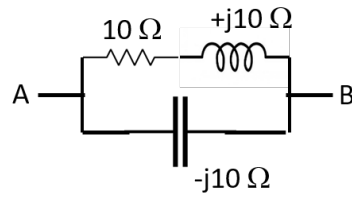

Answer:

$$Z_{AB} = 10 - j10 \, \Omega = 10\sqrt{2} \angle -\frac{\pi}{4} \text{ rad } \Omega.$$

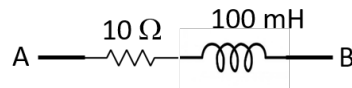
iii. What is Z_{AB} if $\omega = 100 \text{ rad/s}$?



Answer:

$$Z_{AB} = 10 + j10 \, \Omega = 10\sqrt{2} \angle +\frac{\pi}{4} \text{ rad } \Omega.$$

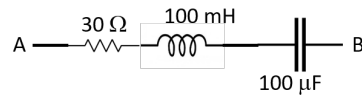
iv. What is Z_{AB} if $f = 50 \text{ Hz}$?



Answer:

$$Z_{AB} = 30 - j0.4 \, \Omega \approx 30 \angle -0.01 \text{ rad } \Omega.$$

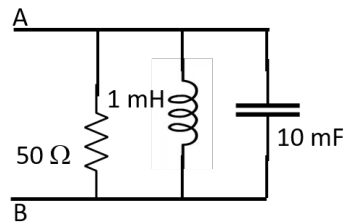v. What is Z_{AB} if $f = 50 \text{ Hz}$?




Answer:

$$Z_{AB} \approx 10 + j20 \, \Omega = 22.36 \angle 1.1 \text{ rad } \Omega.$$


E. Circuit analysis:

E-1. Use phasor and impedance to determine the unknown currents/voltages as indicated in each circuit.

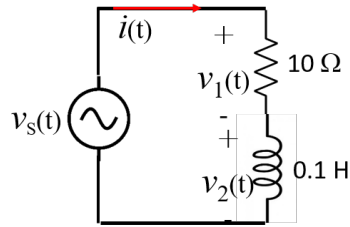
- a. If $v_S = 200 \sin(2\pi 50t)$, find i , v_1 and v_2 . Express your answers as functions of time.



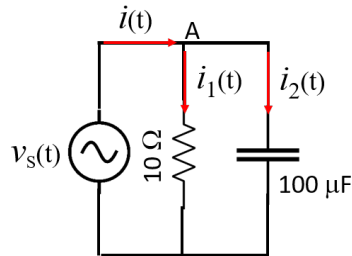- b. In the circuit below, the voltage source is sinusoidal with RMS voltage 71 V and frequency 50 Hz. Determine the RMS values of i , i_1 , and i_2 .



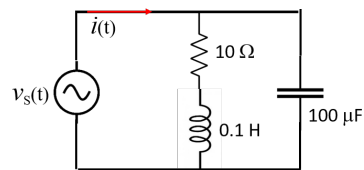- c. In the circuit below source is 50 V (rms) and $\omega = 300$ rad/s. Determine the RMS value of the source current.



Answer:

$$a. i = 6.1 \sin(\omega t - 1.26) \text{ amp}, \quad v_1 = 61 \sin(\omega t - 1.26),$$

$$v_2 = 191 \sin(\omega t + 0.31), \quad \omega = 2\pi \times 50 \text{ rad/s}$$

$$b. I_1 = 7.1 \text{ A}, \quad I_2 = 2.23 \text{ A}, \quad I = 7.44 \text{ A}.$$

$$c. I = 0.5 \text{ A}$$

E-2 A circuit with impedance $Z = 8 + j6 \Omega$ is connected to a sinusoidal voltage source with amplitude of 5V.

- What is the amplitude of the resulting current?
- What is the phase of current waveform with respect to the source voltage?

Answer:

$$a. 0.5 \text{ A}, \quad b. -0.64 \text{ rad}.$$

E-3. An equipment connected to the utility supply 230 V, 50 Hz draws RMS current of 5 A, and the current lags the voltage by $\frac{\pi}{6}$ rad.

- Find the impedance $Z \angle \theta$ of the equipment.

- b. If the impedance is modelled as series connection of two components, determine the values of the individual components.

Answer:

$$a. Z = 46 \angle \frac{\pi}{6} \Omega, \quad b. R = 39.8 \Omega, \quad L = 73 \text{ mH}.$$

- E-4. Determine the frequency (Hz) at which the impedance of a series R-L-C is the smallest if $R = 100 \Omega$, $L = 0.1 \text{ mH}$, and $C = 1000 \mu\text{F}$?

Answer: 503 Hz.