

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

# EE2111A Week 6 Studio 1

## Filters & Tutorials

Ni Qingqing  
NUS, ECE

`ni.qq@nus.edu.sg`

February 17, 2024

# Table of Contents

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

## 1 Learning Objectives

## 2 Review: Wk5S2

- Review: Activity 1
- Review: Activity 2

## 3 Filters

- Intro
- I. Potential Divider
- Gain
- II. RC Low-pass Filter
- More on Gain
- Frequency Response
- Cutoff Frequency
- III. RC High-pass Filter
- IV. RC Bandpass Filter

## 4 Practice Qn. Tut

# Year 1 EE Module Feedback Survey

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain


Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter


IV. RC Bandpass  
Filter

Practice Qn. Tut



**NUS ECE**  
Undergraduate  
Student Council

AY23/24 Sem 2 Course Feedback



<https://forms.office.com/r/Ub1J6gtjqy>

# Learning Objectives

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

We will first revise the following:

- KVL /KCL in AC Circuit.

At the end of this session, you should be able to:

- appreciate how RC and RL filters work.
- design RC/RL filters for given specifications.

# Activity 1: KVL in a series RLC Circuit

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

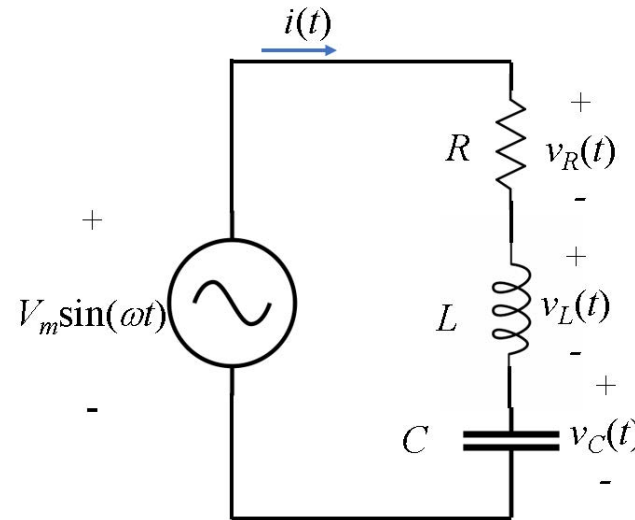IV. RC Bandpass  
Filter

Practice Qn. Tut

Revisit the steps to derive phasor expression of voltages:



- Measure the amplitude of  $v_C(t)$ ,  $v_L(t)$ ,  $v_R(t)$ , and their time shift w.r.t.  $v_S(t)$
- Calculate phase shift w.r.t.  $v_S(t)$  from time shift
- (Optional) Write down time domain expression  $v_C(t)$ ,  $v_L(t)$ ,  $v_R(t)$ , and  $v_S(t)$
- Derive  $\bar{V}_C$ ,  $\bar{V}_L$ ,  $\bar{V}_R$ , and  $\bar{V}_S$
- Verify:  $\bar{V}_S = \bar{V}_C + \bar{V}_L + \bar{V}_R$

# Activity 1: Derive $\bar{V}_R$

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

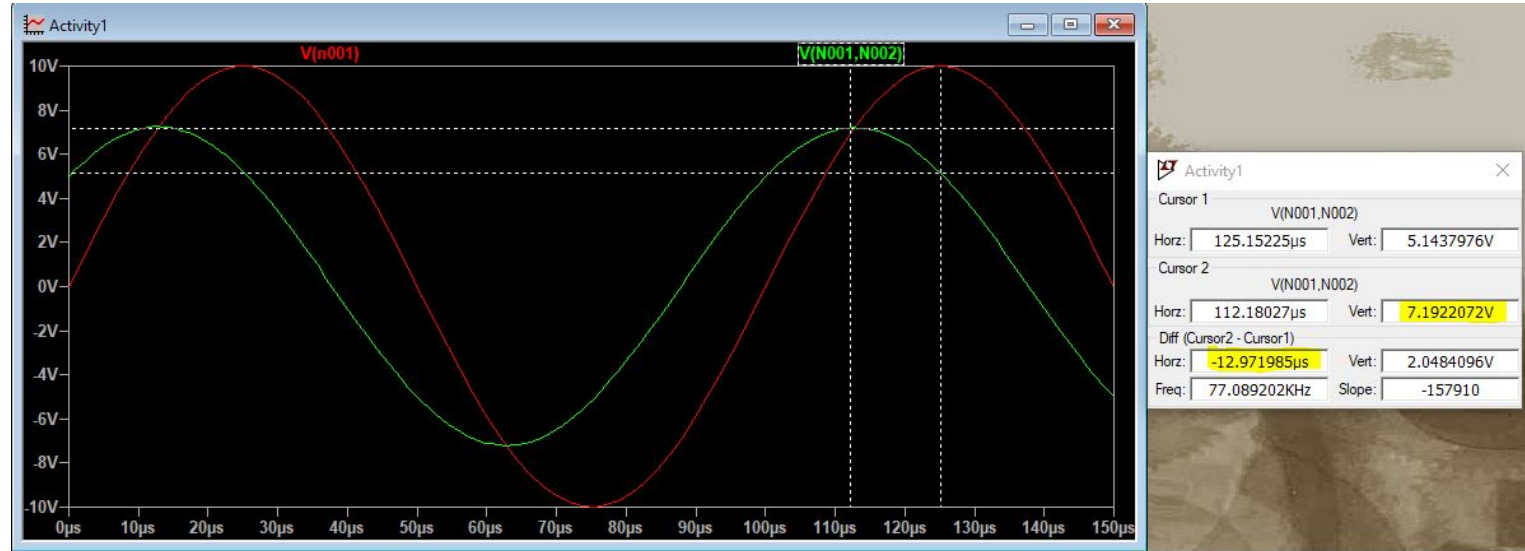IV. RC Bandpass  
Filter

Practice Qn. Tut

Result simulated with LTSpice, Red: Source Voltage,  $V_S(t)$ , Green: Voltage Cross component R/L/C.



- Measurement:  $V_{R,Amp} = 7.19V$ ,  $\Delta t = -12.97\mu s$
- Calculate:  
$$\Delta\phi = \omega\Delta t = 2\pi f\Delta t = 2\pi \times 10kHz \times (-12.97)\mu s = -0.81 \text{ rads}$$
- Since  $V_S$  is the reference signal, it has a phase angle of 0. Comparing to  $V_S$ ,  $V_R$  has a phase shift of  $\Delta\phi = -0.81$  rads. Hence the time domain expression is:

$$v_R(t) = A\sin(\omega t + \phi) = A\sin(\omega t + (0 + \Delta\phi)) = 7.19\sin(\omega t - 0.81)$$

- Derive:  $\bar{V}_R = 7.19\angle -0.81$ ,

# Activity 1: Derive $\bar{V}_C$

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

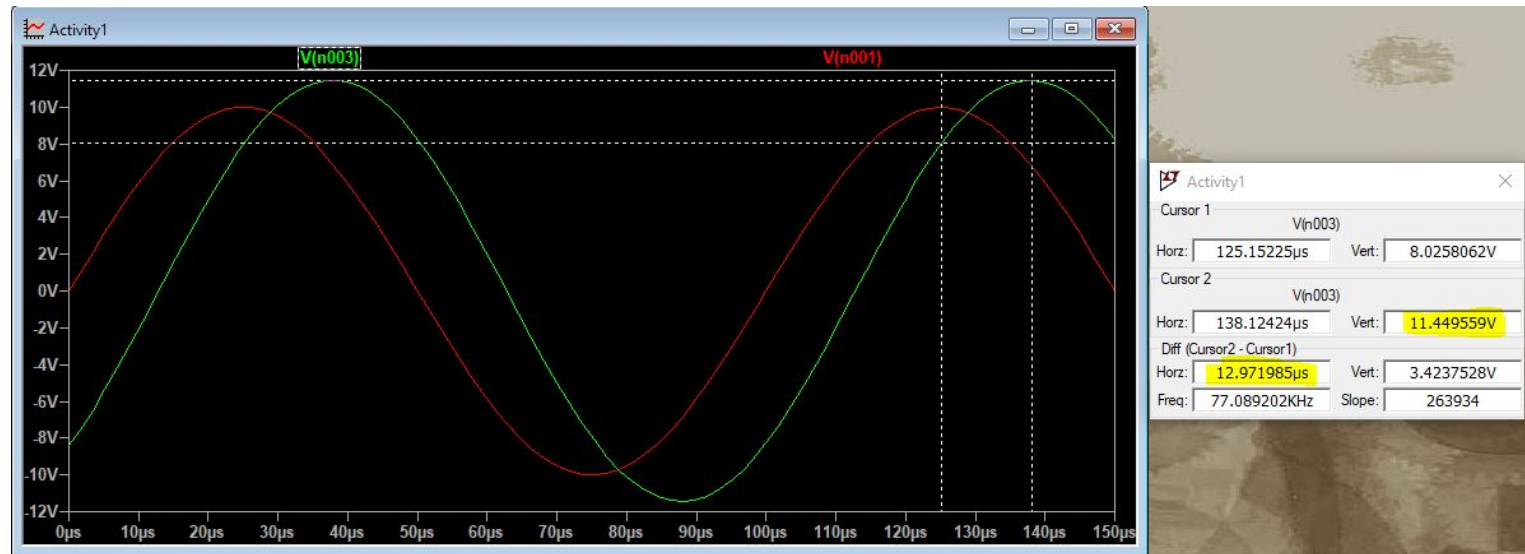IV. RC Bandpass  
Filter

Practice Qn. Tut

Result simulated with LTSpice, Red: Source Voltage,  $V_S(t)$ , Green: Voltage Cross component R/L/C.



- Measurement:  $V_{C,Amp} = 11.45V$ ,  $\Delta t = 12.97\mu s$
- Calculate:  $\Delta\phi = \omega\Delta t = 2\pi f\Delta t = 2\pi \times 10kHz \times 12.97\mu s = 0.81$  rads
- Derive:  $\bar{V}_C = 11.45\angle 0.81$ ,

# Activity 1: Derive $\bar{V}_L$

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

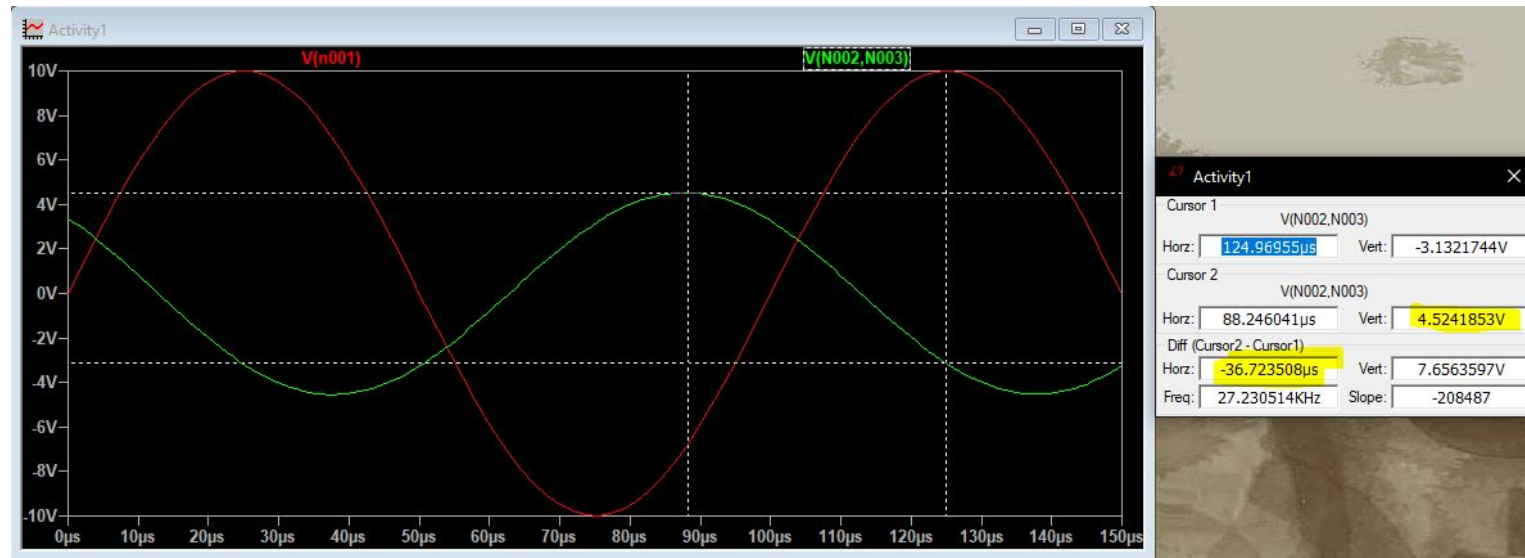IV. RC Bandpass  
Filter

Practice Qn. Tut

Result simulated with LTSpice, Red: Source Voltage,  $V_S(t)$ , Green: Voltage Cross component R/L/C.



- Measurement:  $V_{L,Amp} = 4.52V$ ,  $\Delta t = -36.72\mu s$
- Calculate:  
$$\Delta\phi = \omega\Delta t = 2\pi f\Delta t = 2\pi \times 10kHz \times (-36.72)\mu s = -2.31 \text{ rads}$$
- Derive:  $\bar{V}_L = 4.52\angle -2.31$ ,



# Activity 1: Verify KVL

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

To verify KVL, we want to show that  $\bar{V}_S = \bar{V}_R + \bar{V}_C + \bar{V}_L$ .

- $\bar{V}_S = 10\angle 0$  (Why 0?)
- $\bar{V}_R = 7.19\angle -0.81$
- $\bar{V}_C = 11.45\angle 0.81$
- $\bar{V}_L = 4.52\angle -2.31$
- Can we directly sum them up? You can do so with a calculator!
  - Method 1: convert polar form ( $A\angle\phi$ ) into rectangular form ( $a + jb$ )

$$A\angle\phi = A\cos\phi + jA\sin\phi$$

- Method 2: Set complex display as  $A\angle\phi$  and sum up polar form directly with a calculator!
- $\bar{V}_R + \bar{V}_C + \bar{V}_L = 9.81\angle -0.024 \approx 10\angle 0$

# Activity 2

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

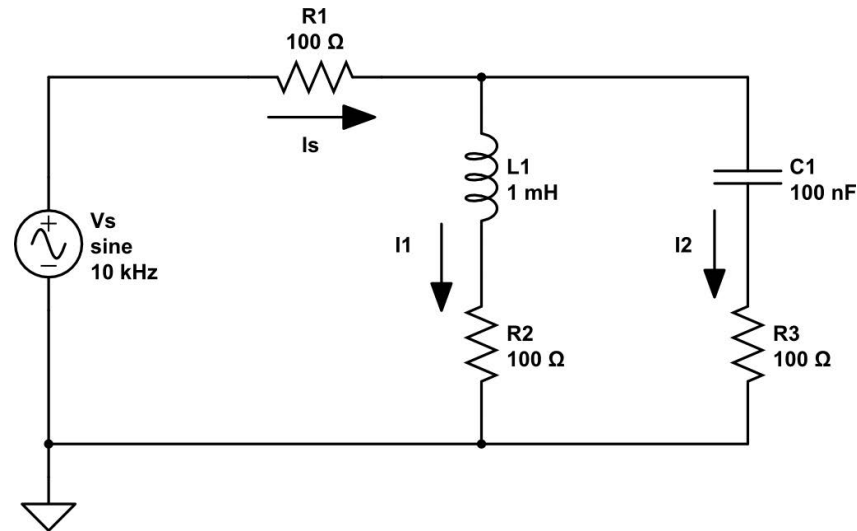IV. RC Bandpass  
Filter

Practice Qn. Tut

Revisit the steps to derive phasor expression of currents:



- Measure the amplitude of  $v_{R1}(t)$ ,  $v_{R2}(t)$ ,  $v_{R3}(t)$ , and their time shift w.r.t.  $v_S(t)$
- Calculate phase shift w.r.t.  $v_S(t)$  from time shift
- Calculate the amplitude of  $i_S(t)$ ,  $i_1(t)$ ,  $i_2(t)$  with Ohm's Law
- Derive  $\bar{I}_S$ ,  $\bar{I}_1$ , and  $\bar{I}_2$
- Verify  $\bar{I}_S = \bar{I}_1 + \bar{I}_2$

# Activity 2: Derive $\bar{I}_1$

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

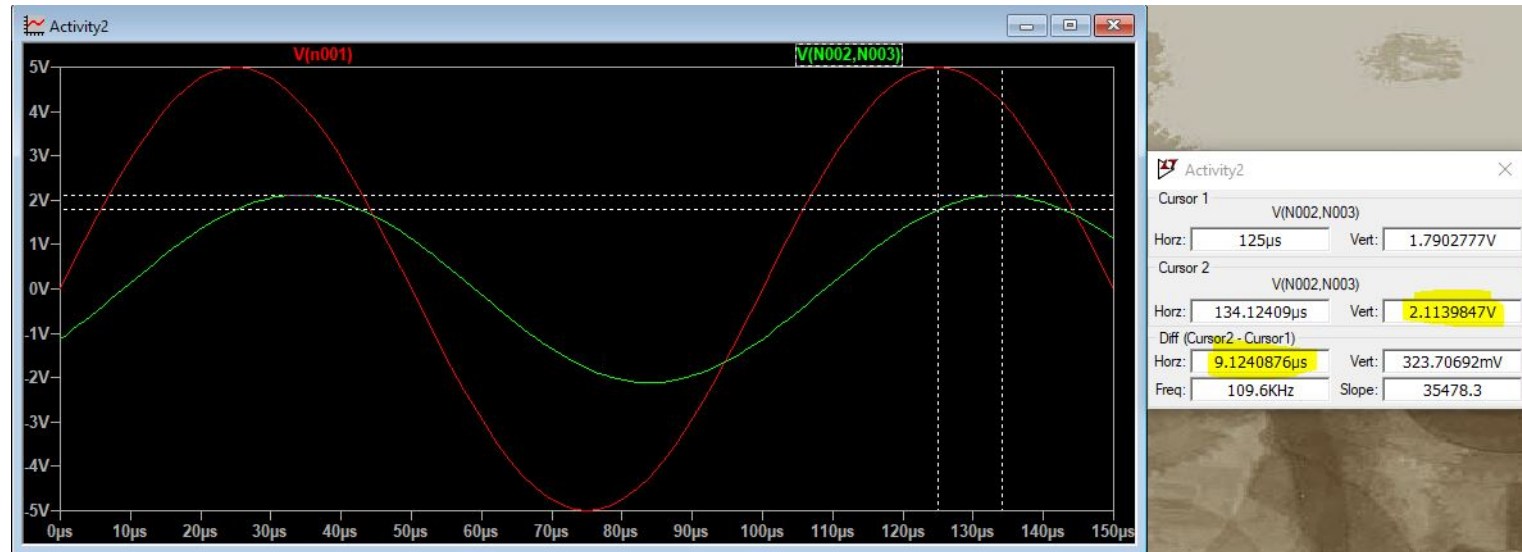IV. RC Bandpass  
Filter

Practice Qn. Tut

Result simulated with LTSpice, Red: Source Voltage,  $V_S(t)$ , Green: Voltage Cross component R/L/C.



- Measurement:  $V_{R2,Amp} = 2.11V$ ,  $\Delta t = 9.12\mu s$
- Calculate:  $\Delta\phi = \omega\Delta t = 2\pi f\Delta t = 2\pi \times 10kHz \times 9.12\mu s = 0.57$  rads
- Calculate:  $I_{1,Amp} = \frac{V_{R2,Amp}}{R2} = \frac{2.11}{100} = 0.0211$  A
- For a resistor, the voltage across it and the current through it is always in phase. Hence, compared to the source voltage,  $I_S$  has a phase shift of 0.57 rads!
- Derive:  $\bar{I}_1 = 0.0211\angle 0.57$

# Activity 2: Derive $\bar{I}_2$

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

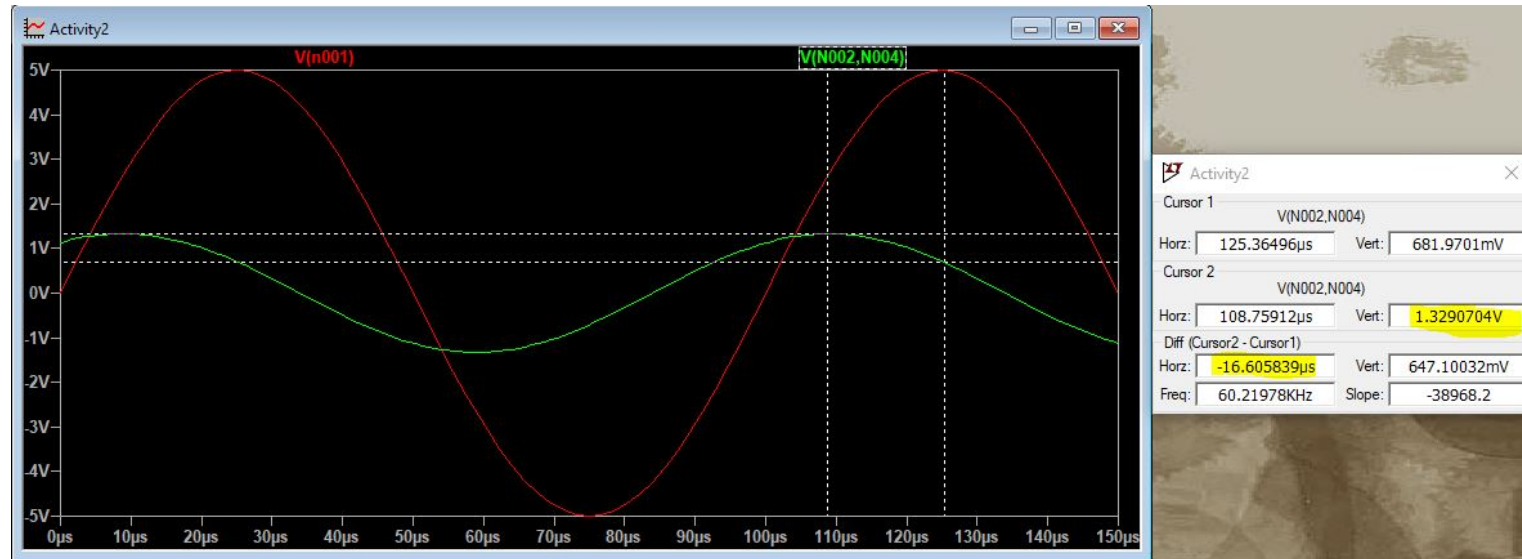IV. RC Bandpass  
Filter

Practice Qn. Tut

Result simulated with LTSpice, Red: Source Voltage,  $V_S(t)$ , Green: Voltage Cross component R/L/C.




- Measurement:  $V_{R3,Amp} = 1.33V$ ,  $\Delta t = -16.61\mu s$
- Calculate:  
$$\Delta\phi = \omega\Delta t = 2\pi f\Delta t = 2\pi \times 10kHz \times (-16.61)\mu s = -1.04 \text{ rads}$$
- Calculate:  $I_{2,Amp} = \frac{V_{R3,Amp}}{R3} = \frac{1.33}{100} = 0.0133 \text{ A}$
- For a resistor, the voltage across it and the current through it is always in phase. Hence, compared to the source voltage,  $I_S$  has a phase shift of  $-1.04$  rads!
- Derive:  $\bar{I}_2 = 0.0133\angle -1.04$

# Activity 2: Derive $\bar{I}_S$

EE2111A Week 6  
Studio 1

Ni Qingqing

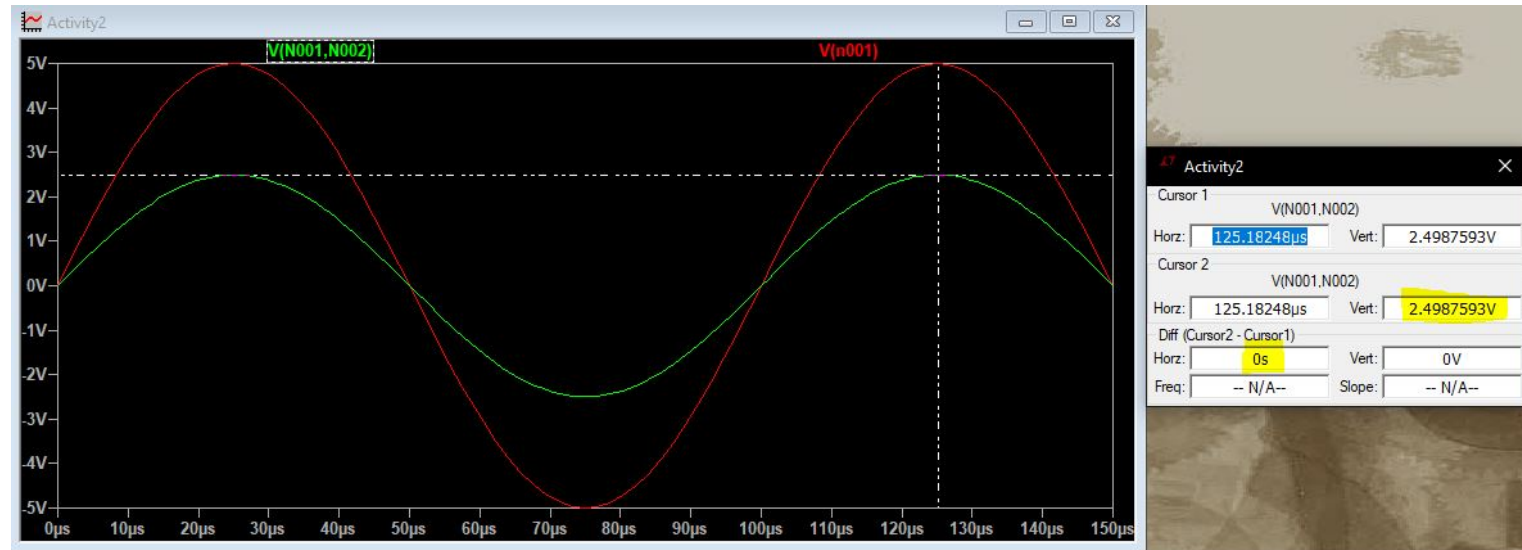Result simulated with LTSpice, Red: Source Voltage,  $V_S(t)$ , Green: Voltage Cross component R/L/C.



- Measurement:  $V_{R1,Amp} = 2.5V$ ,  $\Delta t = 0\mu s$  (?)
- Calculate:  $\Delta\phi = \omega\Delta t = 2\pi f\Delta t = 2\pi \times 10kHz \times 0\mu s = 0$  rads
- Calculate:  $I_{S,Amp} = \frac{V_{R1,Amp}}{R1} = \frac{2.5}{100} = 0.025$  A
- For a resistor, the voltage across it and the current through it is always in phase. Hence, compared to the source voltage,  $I_S$  has a phase shift of 0 rads!
- Derive:  $\bar{I}_S = 0.025\angle 0$ ,

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

# Activity 2: Verify KCL

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

To verify KCL, we want to show that  $\bar{I}_S = \bar{I}_1 + \bar{I}_2$ .

- $\bar{I}_S = 0.025 \angle 0$
- $\bar{I}_1 = 0.0211 \angle 0.57$
- $\bar{I}_2 = 0.0133 \angle -1.04$
- $\bar{I}_1 + \bar{I}_2 = 0.024 \angle -0.0034 \approx 0.025 \angle 0$

# Can you tell that this circuit is resonating?

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

- When resonating, the complex circuit is equivalent to a pure resistive circuit.
- In a pure resistive circuit, the Voltage source and Voltage across a resistor are always in-phase.
- In a mixed circuit with R, L, and C, the Voltage source and Voltage across a resistor are **USUALLY** out-of-phase. The exception happens when the circuit is at **resonance**.
- What's the equivalent R of the Activity 2 circuit?

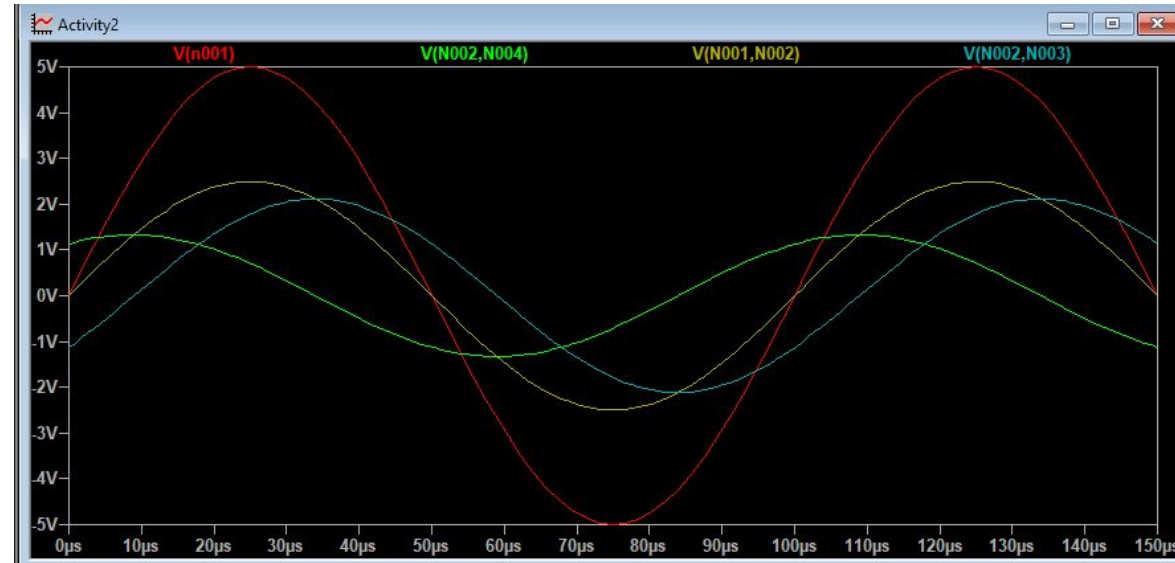


Figure 1: Red:  $V_S$ , Green:  $V_{R2}$ , Yellow:  $V_{R1}$ , Blue:  $V_{R3}$

# What is a filter

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

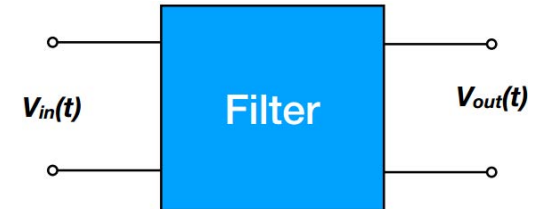IV. RC Bandpass  
Filter

Practice Qn. Tut

A filter is a **2-port** device that **takes in** a signal  $V_{in}(t)$  at the input port, **modifies** it in some way, and **sends out** the modified signal  $V_{out}(t)$  on the output port. Signals are often simply time-varying voltages.



Today, we will go through four basic filters:

- Potential Divider as a Filter
- RC Low-pass Filter
- RC High-pass Filter
- Bandpass Filter

And characterize filters with:

- Gain
- Cutoff Frequency
- Frequency response (Bode Plot)



# Potential Divider as a Filter

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

For this potential divider circuit:

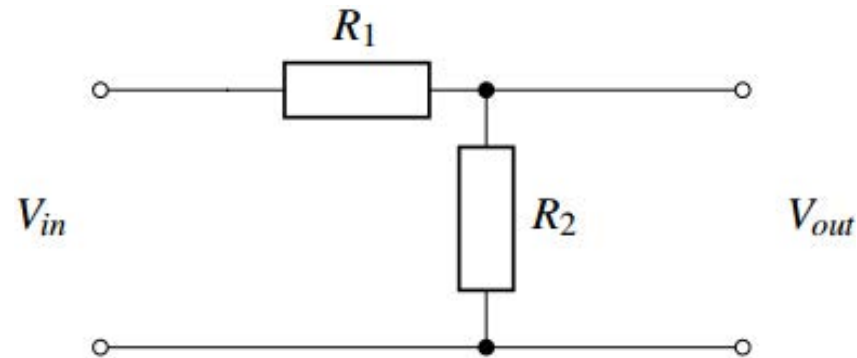

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

So the output signal is simply a **scaled** version of the input signal.

If the input signal is time-varying, the output signal will also vary with time:

$$V_{out}(t) = \frac{R_2}{R_1 + R_2} V_{in}(t)$$

In the expression:

$$V_{out}(t) = \frac{R_2}{R_1 + R_2} V_{in}(t)$$

The scaling factor  $G$  is what we call the Gain of the filter.

$$V_{out}(t) = GV_{in}(t)$$

$$G = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

Notice that:

- The gain quantifies the ratio between the output signal and input signal, it takes value from the range of  $(0, +\infty]$ 
  - When  $G < 1$ , the output signal has a smaller amplitude compared to the input signal
  - When  $G > 1$ , the output signal has a greater amplitude compared to the input signal
  - When  $G = 1$ , the input and output signals have the same amplitude.
- The gain  $G$  here is **independent** of the input signal. This is **not** generally the case for other circuits.

# RC Low-pass Filter I

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

For this RC circuit:

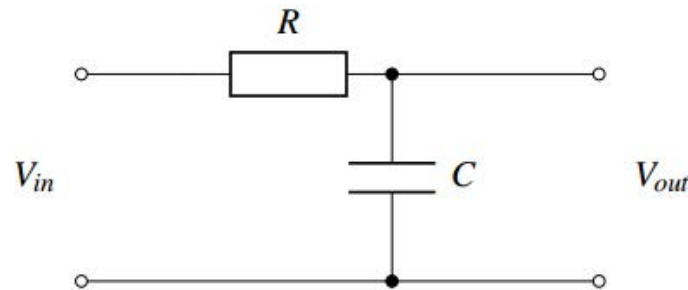

- If  $V_{in}$  is not time-varying (DC signal),  $C$  serves as an open circuit:
  - $C$  will initially charge up to  $V_{in}$  through  $R$ .
  - Once  $C$  is fully charged, it acts like an open circuit, no current flows through  $C$ .
  - At this point, there is no current flow through the  $R$  as well, and there is no voltage drop across  $R$
  - In the steady-state:

$$V_{out} = V_{in}$$

# RC Low-pass Filter II

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain


Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

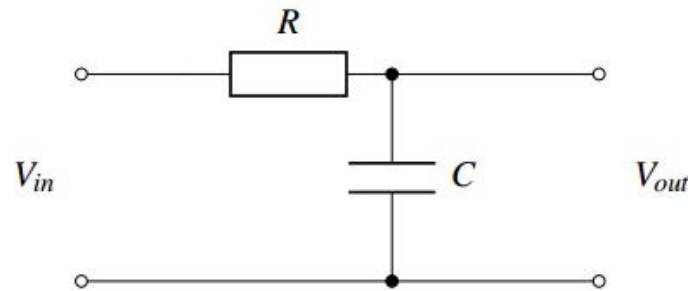

- If  $V_{in}$  is time-varying (AC signal), we can analyze this AC circuits:
  - Let the angular frequency,  $\omega = 2\pi f$
  - Let the impedance of  $R$  and  $C$  be  $Z_R$  and  $Z_C$  respectively.
  - Let  $\bar{V}_{out}$  and  $\bar{V}_{in}$  be the phasor of output and input signal
  - The complex gain  $\bar{G}$ :

$$\bar{G} = \frac{\bar{V}_{out}}{\bar{V}_{in}} = \frac{Z_C}{Z_R + Z_C} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

# Complex Gain? Gain?

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

We've derived the expression of the **Complex Gain** of the RC Low-pass filter earlier.

However, when referring to **Gain**, we usually mean the **magnitude of Complex Gain**,  $|G|$ . It can be found by taking the modulus of  $\bar{G}$ .

For a complex number  $z = a + jb$ , the modulus is given by  $|z| = \sqrt{a^2 + b^2}$ .

$$\begin{aligned}|G| &= \left| \frac{1}{1 + j\omega RC} \right| = \frac{|1|}{|1 + j\omega RC|} \\ &= \frac{1}{\sqrt{1^2 + (\omega RC)^2}} \\ &= \frac{1}{\sqrt{1 + (\omega RC)^2}}\end{aligned}$$

You can use the calculator "Abs" or " $|\square|$ " function to calculate  $|G|$ .

We have now derived  $|G|$  as a ratio between  $V_{out}$  and  $V_{in}$ .

But usually, we would like to express Gain in the unit of decibels (dB).  
To convert  $|G|$  into  $G_{dB}$ :

$$G_{dB} = 20 \log_{10}(|G|)$$

Representing gain as a ratio:

- When  $|G| < 1$ , amplitude of output signal smaller than input signal
- When  $|G| > 1$ , amplitude of output signal greater than input signal
- When  $|G| = 1$ , amplitude of output signal equals to input signal

Representing gain in dB:

- When  $G_{dB} < 0$ , amplitude of output signal smaller than input signal
- When  $G_{dB} > 0$ , amplitude of output signal greater than input signal
- When  $G_{dB} = 0$ , amplitude of output signal equals to input signal


With  $G_{dB}$ , we are using 0 to gauge amplification and suppression, we can avoid values like 0.0001 or 10000. Which also helps with better Frequency Response plotting.

# Frequency Response of filter in $|G|$ and $G_{dB}$

You should notice that the gain of RC low-pass filter depends on the frequency of the input signal, as  $\omega$  is part of the term.


Let's plot  $|G|$  and  $G_{dB}$  against the input signal frequency respectively:

$|G|$  vs. frequency

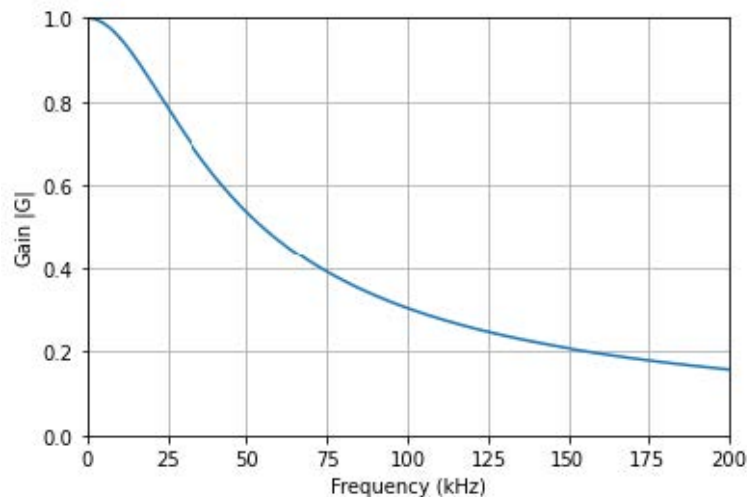

$f$  is in linear scale

$G_{dB}$  vs. frequency

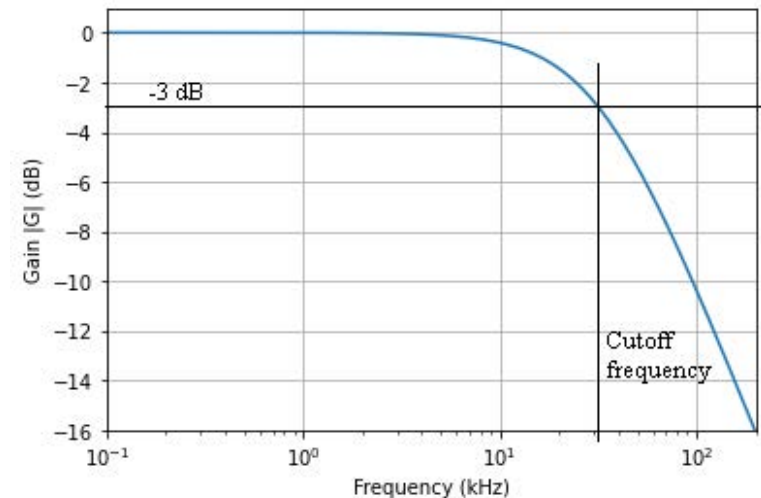

$f$  is in logarithmic scale

As you can see, the filter allows low frequencies to pass through and attenuates the high frequencies.

$$R = 1\text{ k}\Omega, C = 5\text{ nF}$$

# Frequency Response of filter in $|G|$ and $G_{dB}$ II

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

In both plots, we plotted the exact same thing, but which one is preferred?

*To an electrical engineer, the Bode Plot (the one on the right) is preferred!*

## Bode Plot

- In a logarithmic scale, multiples have the same distance. (e.g.: doubling: the distance 30 to 60 matches the distance 40 to 80 and 100 to 200).
- logarithmic scales are useful where arithmetic ratios are more significant than arithmetic differences.
- Also, in logarithmic scales, we have the lower frequency region expanded, and higher frequency compressed, this would give us a better view over a large range of frequencies while still being able to observe the frequency response trend properly.



# Cutoff Frequency: -3dB

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

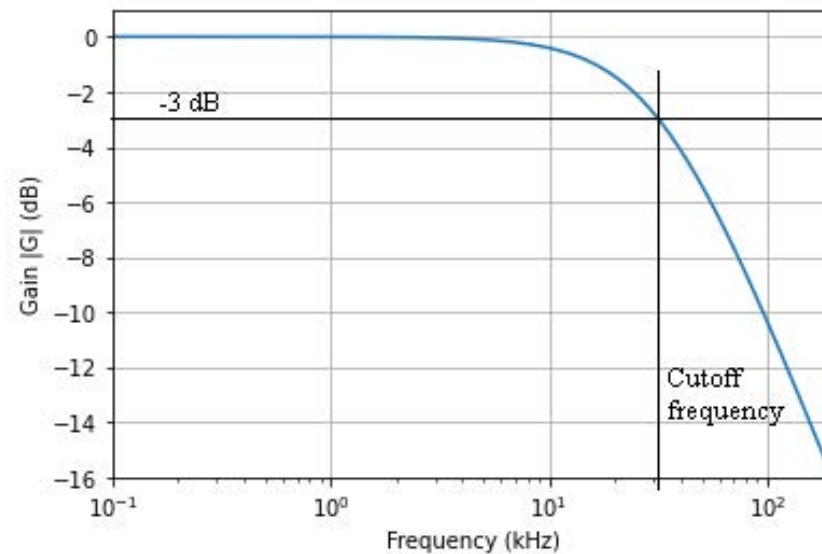IV. RC Bandpass  
Filter

Practice Qn. Tut

In the frequency response plot below, one particular point is marked:



At a particular input signal frequency, the response drops to -3dB.

In linear scale, it means that the output signal amplitude is equal to the input signal amplitude scaled by a factor of 0.707.

This particular input frequency is known as the **cutoff frequency**.

$$f_{cutoff} = \frac{1}{2\pi RC}$$

# Frequency Response: Bode Plot

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

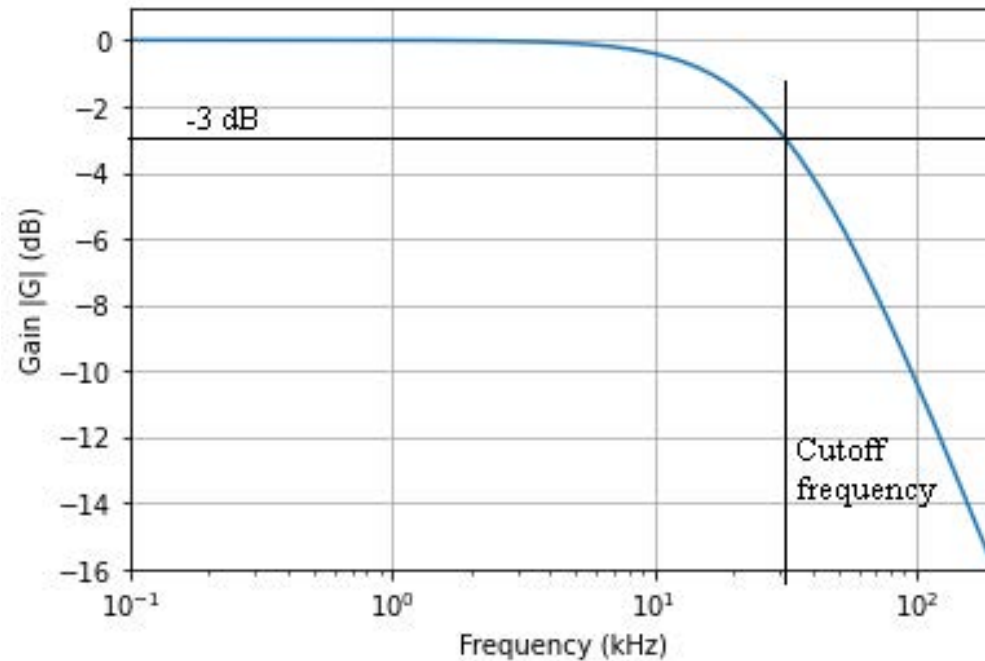IV. RC Bandpass  
Filter

Practice Qn. Tut

In the frequency response plot below, you may find all the information needed for a filter:



- Gain at each input frequency
- Cutoff Frequency (-3dB point)
- Attenuation effectiveness (roll-off gradient) (Not examinable)

# RC High-pass Filter I

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

For this RC circuit:

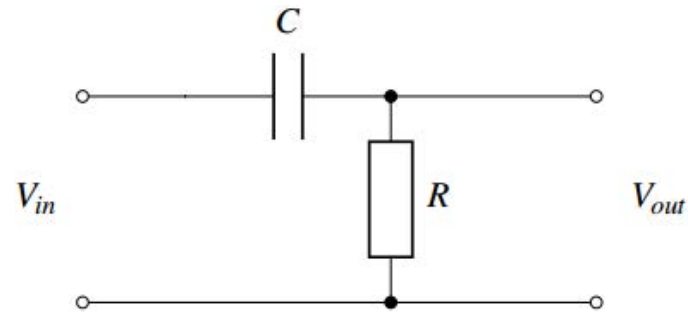

- If  $V_{in}$  is not time-varying (DC signal),  $C$  serves as an open circuit:
  - $C$  will initially charge up to  $V_{in}$  through  $R$ .
  - Once  $C$  is fully charged, it acts like an open circuit, no current flows through  $C$ .
  - At this point, there is no current flow through the  $R$  as well, and there is no voltage drop across  $R$ .
  - In the steady-state:

$$V_{out} = 0V$$

# RC High-pass Filter II

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain


Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

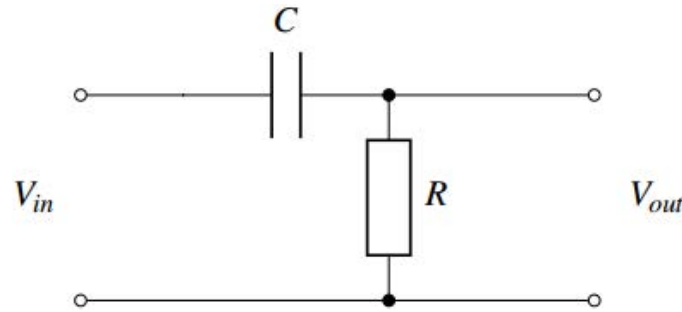

- If  $V_{in}$  is time-varying (AC signal), we can analyze this AC circuits:

- Let the angular frequency,  $\omega = 2\pi f$
- Let the impedance of  $R$  and  $C$  be  $Z_R$  and  $Z_C$  respectively.
- Let  $\bar{V}_{out}$  and  $\bar{V}_{in}$  be the phasor of output and input signal
- The complex gain  $\bar{G}$ :

$$\bar{G} = \frac{\bar{V}_{out}}{\bar{V}_{in}} = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

- The gain  $|G|$ :

$$|G| = \frac{j\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

# High-pass filter Frequency Response

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response


Cutoff Frequency

III. RC High-pass  
Filter

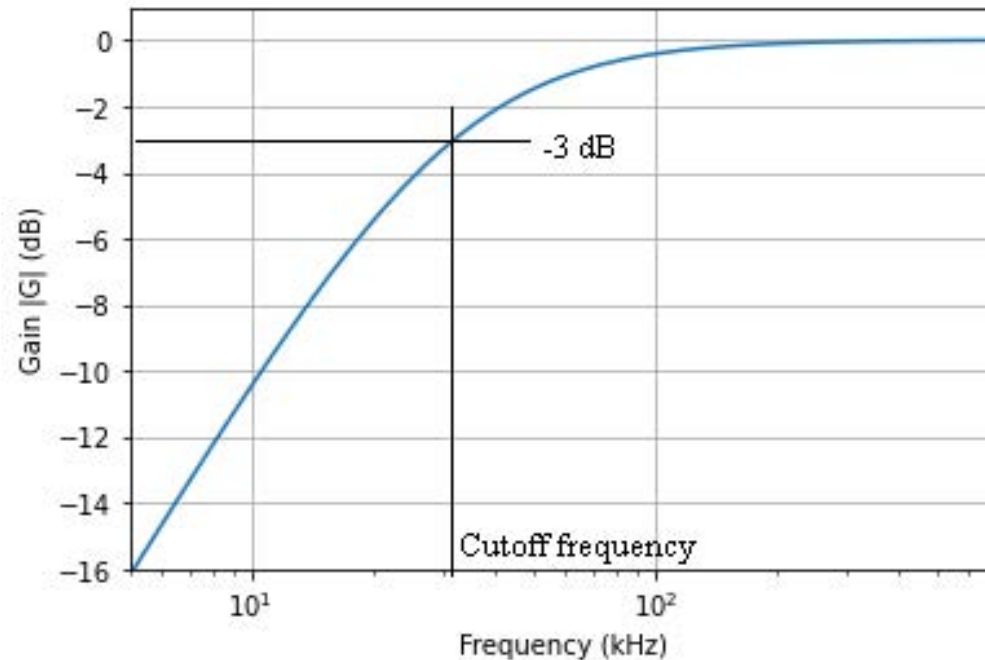IV. RC Bandpass  
Filter

Practice Qn. Tut

Let's plot the frequency response of this high-pass filter:



As you can see, the filter allows high frequencies to pass through and attenuates the low frequencies.


The cutoff frequency remains the same:

$$f_{cutoff} = \frac{1}{2\pi RC}$$

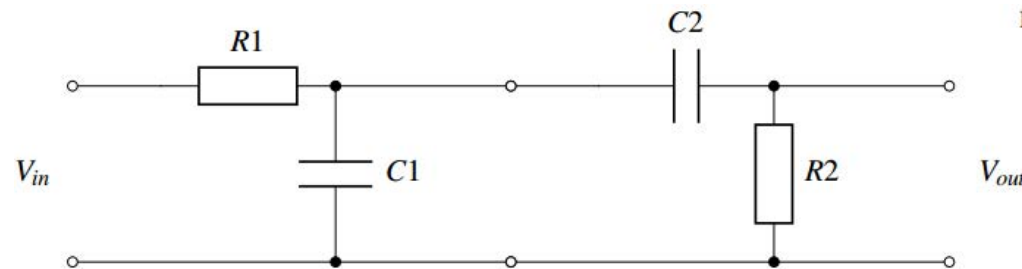
# RC Bandpass Filter

If we want a filter that only allows frequencies between  $f_1$  and  $f_2$  to pass through, we can combine a RC high-pass filter with a RC low-pass filter.

Such filters are called **band-pass** filters.



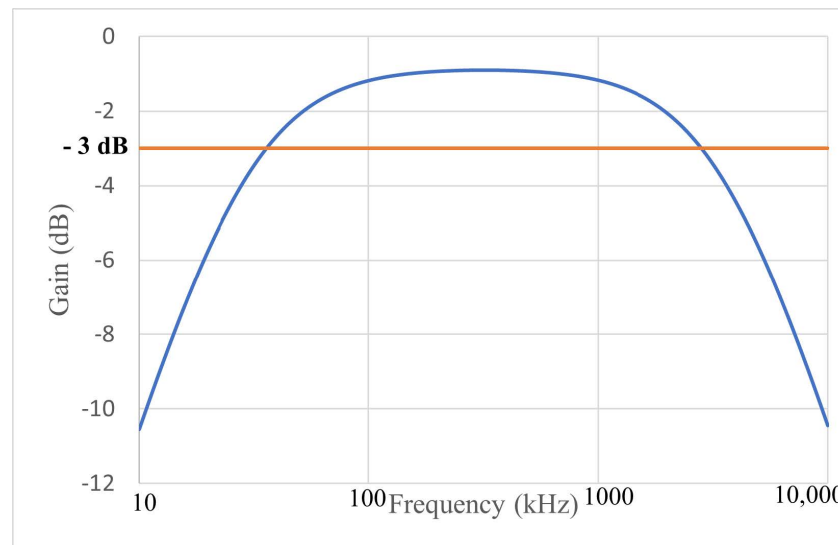Which has a frequency response like shown below:



The difference  $f_2 - f_1$  is known as the **bandwidth** of the filter. Such filters have two cutoff frequencies.

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

We will go through some practice questions and the quiz questions.  
Organized notes will be uploaded after the class within 2 days.

EE2111A Week 6  
Studio 1

Ni Qingqing

Learning  
Objectives

Review: Wk5S2

Review: Activity 1

Review: Activity 2

Filters

Intro

I. Potential Divider

Gain

II. RC Low-pass Filter

More on Gain

Frequency Response

Cutoff Frequency

III. RC High-pass  
Filter

IV. RC Bandpass  
Filter

Practice Qn. Tut

Thank You  
Any questions?